



Electrical Engineering
Indian Institute of Technology Hyd
Analog Electronics

March 9, 2024

Deadline: 16 March 2024

Assignment # 4

Maximum Marks: TBD

Instructions:

1. Use LT spice software.
-

1. Design the following in LT Spice:
 - a. A RC phase shift oscillator (3 stage) for 50 kHz sin wave signal output.
 - b. A Wien bridge oscillator for 50 kHz sin wave signal output.
 - c. A Square wave generator for a fundamental frequency of 10 kHz signal output. Use an integrator and convert the square wave signal into triangular wave.
 - d. A Square wave generator for a fundamental frequency of 10 kHz signal output. Use an integrator and convert the square wave signal a sawtooth wave with rise time = 1/2 fall time.
 - e. Design a schmitt trigger circuit and show the hysteresis curve with V_{th} (+ and -ve) = $\pm 200\text{mV}$