



Electrical Engineering
Indian Institute of Technology Hyd
Analog Electronics

March 9, 2024

Deadline: 23 March 2024

Assignment # 5

Maximum Marks: TBD

Instructions:

1. Lab experiments.
-

1. Design the following in LT Spice:

- a. Design a practical integrator using opamps available in the lab. Find the UGB of the opamp and based on the same design the integrator for minimum frequency of 5 kHz. Please mind that for a practical integrator, the minimum frequency of the input signal must be at least 10 times than the cut-off frequency of the system. Choose the passive components wisely to achieve the proper response. Apply a square waveform to this integrator with a time period of 100 us and demonstrate the working of the integrator.

- b. Design a practical differentiator using the same opamp for input signals with frequency ranging from DC to 10 kHz. To realized the system, keep a series resistor with the forward capacitor and keep a capacitor in parallel with feedback resistor.

Please mind that for a practical differentiator, the maximum frequency of the input signal must be at least 10 times lesser than the cut-off frequency of the system. Choose the passive components wisely to achieve the proper response. Plot the frequency response of the differentiator. Apply a sinusoidal waveform of 1 kHz to this system and demonstrate the working of the differentiator.

- c. Use the appropriate components available in the lab and design a 5 bit R-2R ladder DAC on bread board and show the working of the same. Put a reference voltage of 2 volts.